

Open Source Rover

Electrical Assembly Instructions



Jet Propulsion Laboratory
California Institute of Technology

Contents

1 Overview	3
1.1 Tools Necessary	5
1.2 Component Descriptions	6
1.2.1 Battery	6
1.2.2 Voltage Regulators	6
1.2.3 Raspberry Pi 3	6
1.2.4 Printed Circuit Boards	7
1.2.5 LED Matrix	7
1.2.6 Motors	7
1.2.7 Encoders	8
2 Powering Components	8
2.1 Battery Connectors, Switch, and Volt Meter	9
2.2 Volt Meter and Voltage Regulator	12
2.3 Powering the Raspberry Pi	15
2.4 Serial Communication	16
3 Connecting Motors/Encoders	22
3.1 Drive Motors	24
3.2 Corner Motors/Encoders	26
4 Connecting the LED Matrix	30

1 Overview

First it is important to look at the components used in the rover and understand both the data transmission and power system for the rover. Figure 1 shows how each of the electrical components and boards receive power, and Figure 2 shows how data is sent from each of the electrical systems and what communication protocol it uses.

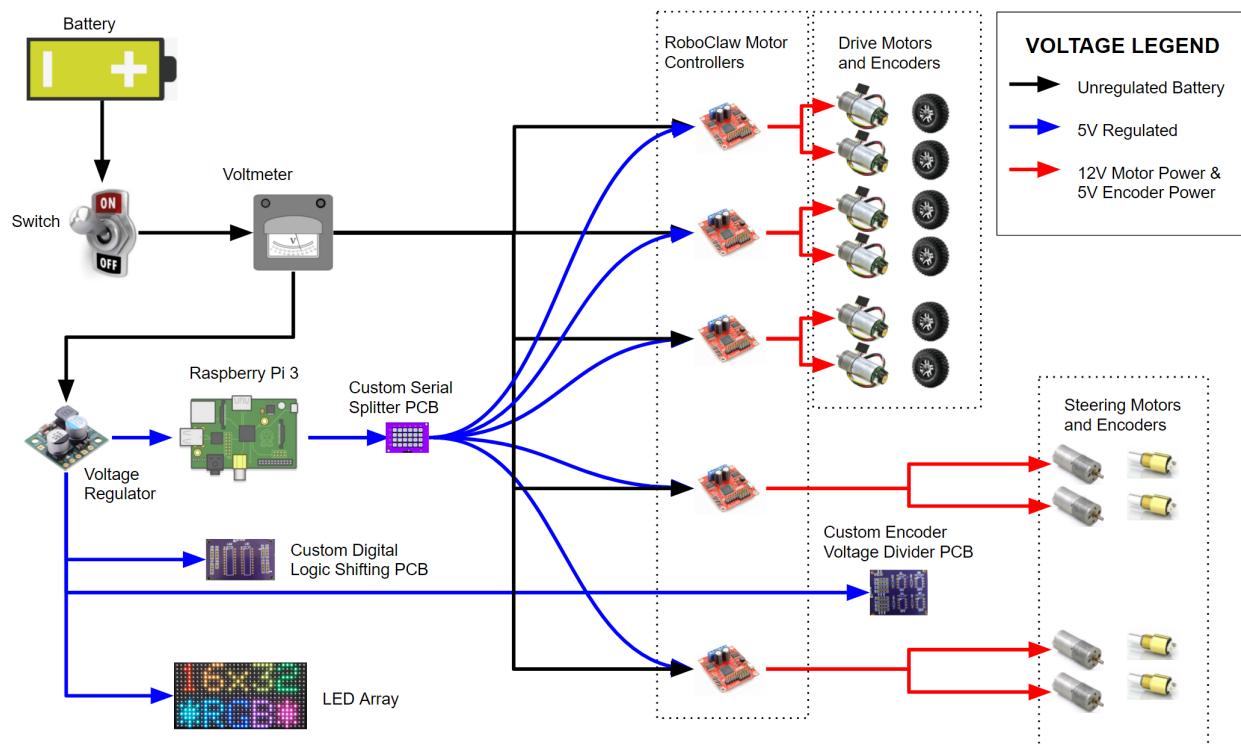


Figure 1: Electrical Power Overview

A few things to note from this is that there are multiple different voltages in the system, there is the unregulated voltage coming from the battery, 5V regulated coming from a voltage regulator, and the 12V motor voltage being sent from the motor controllers to the motors.

1 OVERVIEW

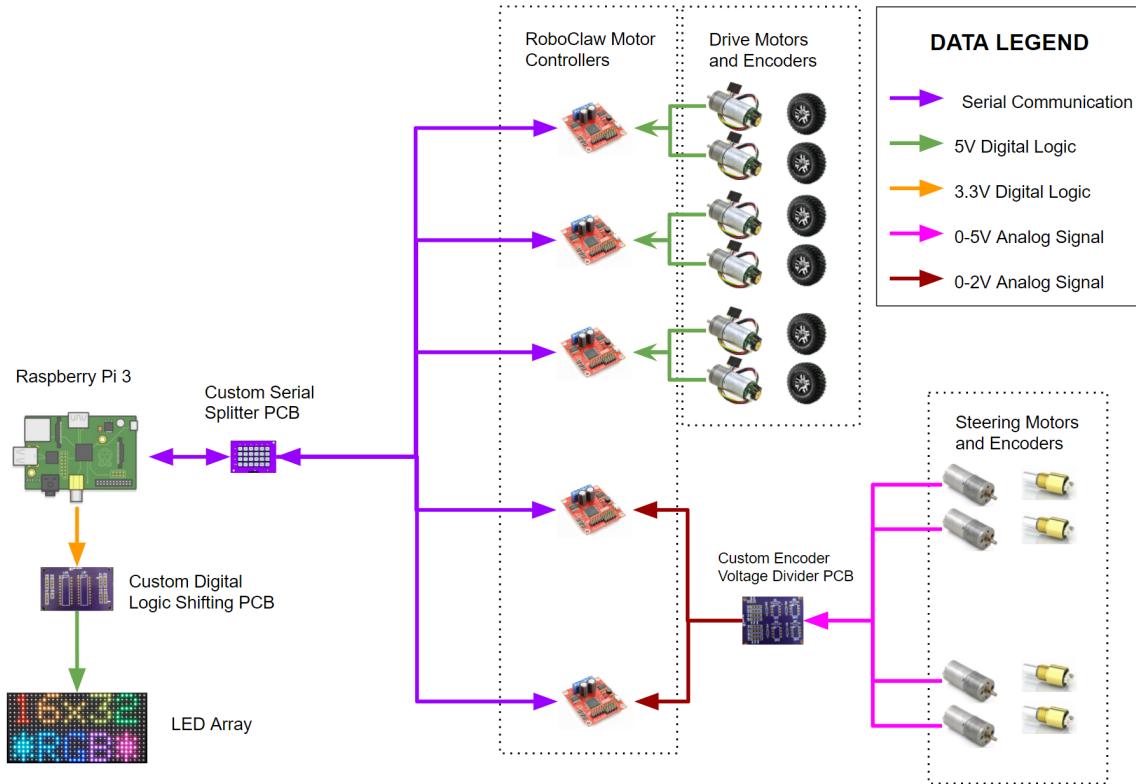


Figure 2: Electrical Data Overview

For the data transmission there is the use of both a 3.3V and 5V digital logic system, analog signals of different max voltages, and Serial communication between devices. Information on these can be found at:

- https://en.wikipedia.org/wiki/Serial_communication
- <https://learn.sparkfun.com/tutorials/analog-vs-digital>

Part	Description
Battery	Provides power to the system. Has an unregulated voltage range of around 11.5V - 16.75V depending on it's charge level
Switch	Mechanical disconnect of the electrical power to the rest of the robot
Volt Meter	Monitors and displays information such as current draw, voltage level, and power consumption of the robot
Voltage Regulator	Takes in the unregulated battery voltage and outputs a steady regulated voltage of 5 volts for consumption of electronics.
Raspberry Pi 3	Acts as the brains and processing power of the robot
LED Matrix	Gives a display to the robot
Motor Controllers	Send voltage signals to the motors as to direction/speed to spin at, and read encoder data
Encoders	Monitors the spinning of the motor to give data like speed and position
Custom PCBs	Single purpose boards made custom for this project, each of which will be explained later on in this document.

1.1 Tools Necessary

Tools Necessary

Item	Image	Item	Image
Heat Shrink Gun		Solder	
Digital Multimeter		Solder Wick	
Solder Iron		Power Supply (optional)	

Figure 3

This project assumes you have some basic electronics components shown in Figure 3. These will all be used in the construction and testing/debugging of this project. Most of these can be purchased inexpensively though digikey or amazon.

1.2 Component Descriptions

The following are brief descriptions and notes about some of the components used. For more information on each you should consult the data sheet for each respective component.

1.2.1 Battery

The battery is used to power all the electrical components, and the motors for this project. The biggest driving factor for battery selection was safeness of the battery while keeping able to drive the current and voltage necessary for operation of all the electronics (we'll go into operating specs more later). The recommended battery was chosen because of it's Poly Switch and PCB protection. These limit the amount of current that can be pulled from the battery, as well as giving protection against things like electrical shorts, and overcharging/fully discharging the battery.

1.2.2 Voltage Regulators

As the battery selected outputs unregulated voltage based on it's charge level voltage regulators are added to give steady DC voltage power to the electronics components. There is a 5V regulator that runs the raspberry pi and the LED matrix, and a 12V regulator that will supply power to the motors which run on 12Volts.

1.2.3 Raspberry Pi 3

The Raspberry Pi 3 Model B was selected as the "brain" of the project. It was chosen for its capability of adding projects and modules to the robot, as it is the most widely developed on open source platform in the world right now. Model B was selected as it comes with the

wifi and bluetooth modules built into the board and don't need external devices for them, allowing the user all 4 USB ports for addons and plug-ins to the project.

1.2.4 Printed Circuit Boards

In order to help with the electronics of this system we designed a few single purpose Printed Circuit Boards (PCBs). In total there are three boards, which are for the following:

Board	Description/Purpose
Voltage Divider	Distributes the +5V and GND to power the absolute encoders. Then takes the 0-5V signal from the encoders and transforms it to a 0-2V signal output
Logic Shifter	Takes the 3.3V digital signals from the raspberry pi and converts them to a 5V digital signal output
Serial Splitter	Splits out the TX/RX serial read/write lines as well as the +5V and GND power pins from the Raspberry Pi and distributes them to each motor controller.

1.2.5 LED Matrix

The LED Matrix gives a 16x32 pixel display, controlled through the raspberry pi. In order to integrate this we followed along with an Adafruit project (but added our own custom PCB which isn't in this tutorial) which can be found at: ¹

- <https://learn.adafruit.com/connecting-a-16x32-rgb-led-matrix-panel-to-a-raspberry-pi/overview>

1.2.6 Motors

Motors are used to do the mechanical movement of the robot. There are many types of motors that exist, in this project we will be used brushed DC motors. More information on

¹This project extension uses a lot of GPIO pins and might want to be swapped out for a different set of devices.

2 POWERING COMPONENTS

motor types and specifically how a brushed DC motor works can be found at the following links:

- https://en.wikipedia.org/wiki/Brushed_DC_electric_motor
- https://en.wikipedia.org/wiki/Electric_motor

1.2.7 Encoders

Encoders are used to get readings on positions and speed of motors as they spin. There are two types used in this project, absolute and quadrature. An absolute encoder is used to get the position of the motor on a fixed scale such that you always know the position even after power cycling the system. This type of encoder will usually have one output, which will either be a PWM digital signal, or an analog signal, each of which will have a specific reading corresponding to the fixed position scale. These are typically more expensive than their quadrature encoder counterparts, which will sense position only relative to the last time the power was cycled or the signal was reset. Quadrature encoders use two digital signals and will look at the different between the signals to sense movement, more information about quadrature encoders can be found at:

- http://www.dynapar.com/Technology/Encoder_Basics/Quadrature_Encoder/

In this project absolute encoders will be used on the corner wheels to get absolute measurements on where the wheels are turned, and quadrature encoders are used at each of the driving wheels to get speed measurements.

2 Powering Components

Here we will be setting up the connections to the electrical components. It is recommended that you try hooking up each of these components outside of the robot body first to test in an easier environment, as well as make sure you fully understand how all the signals are

2 POWERING COMPONENTS Battery Connectors, Switch, and Volt Meter

passed around etc. This guide also assumes that you have already followed the PCB Testing guide and that you have fully tested and functioning PCBs already.

When connecting any of the power lines it is important to consider how much current will be running through that wire, and select the appropriate wire gauge to handle that current. For more information on wire gauge selection you can follow this link:

- https://www.bluesea.com/support/articles/Circuit_Protection/1437

During this project you will need to cut, strip wires, and solder them to extend and split electrical connections. It is important to understand how to do this safely such that you are protecting your system from electrical shorts. Below are a few quick bits of information on these, however make sure to fully understand these processes before proceeding.

- <https://learn.sparkfun.com/tutorials/working-with-wire/how-to-strip-a-wire>
- <https://www.wikihow.com/Splice-Wire>
- <https://www.youtube.com/watch?v=Y8wjjv6lj5KU>

****Note** Please read through this entire section and understand it before starting to connect devices and electronics together.**

2.1 Battery Connectors, Switch, and Volt Meter

We'll start with the battery and connecting it through the switch and volt meter. Figure 4 shows the section of the power diagram we'll be working on, with components and connections made in this section in **RED**.

2 POWERING COMPONENTS

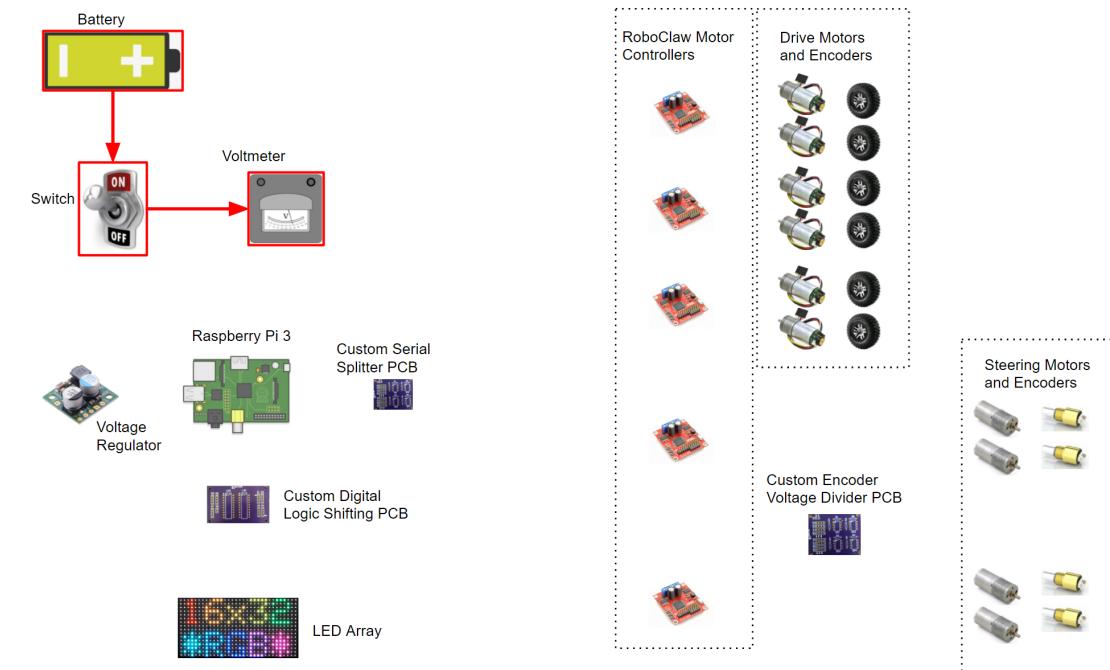


Figure 4: Battery section Overview

Using the Tamiya connectors connect the battery to the switch and then the volt meter following Figure 5. The connectors are to be able to disconnect the battery from the rest of the system so you can charge the battery.

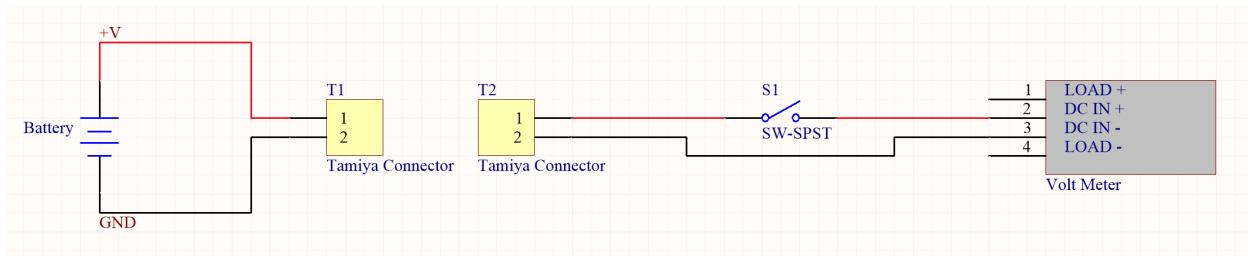


Figure 5: Battery connection through switch and volt meter

2 POWERING COMPONENTS Battery Connectors, Switch, and Volt Meter

There are a couple of very important things to make sure as you are doing this, as with any project where you are working with batteries or electrical current:

The battery **IS LIVE AT ALL TIMES**. This means that at any point if the two terminals of the battery come in contact they will cause an electrical short. This will trigger the protection circuit in the battery, but we do not want to rely on that for safety. Make sure to keep the terminals of the +V and GND separated at all times with no possibility of contact.

The connectors will only fit together in one way. That means you have to make sure your connections are right the first time when soldering them in, make sure to verify this before connecting anything to the battery.

The switch picked out is a Single Pole - Single Throw switch. This means that either the two terminals are connected together in one switch position or there is a physical disconnect when the switch is in the other position. Make sure to test the switch and know which is the ON and OFF positions for the switch previous to connecting it to anything.

It is extremely important to plug the battery in the correct direction into the volt meter as well, as plugging it in backwards could damage the volt meter.

The battery will live in the body of the rover above the electronics plate, with the switch mounting to any of your choice of the 0.5 in holes in the body, and the volt meter has a press fit cutout in the back panel. Figure 6 shows an example of how we installed the switch, and the volt meter/ tamiya connectors. Note how the connectors are, this allows us to unplug the battery and charge it without removing anything.

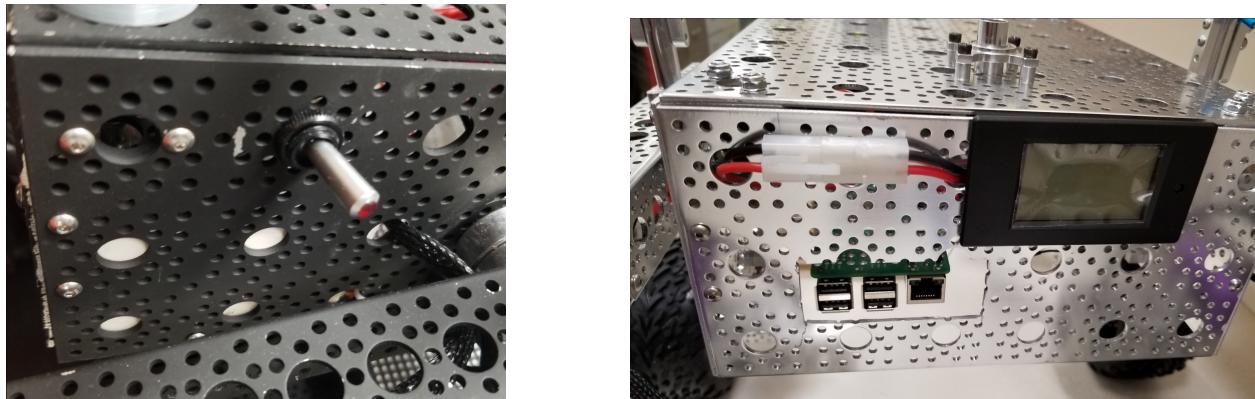


Figure 6: Installing the switch and voltmeter

2.2 Volt Meter and Voltage Regulator

Next is connecting the output side of the volt meter to the 5V voltage regulator and the motor controllers. Figure 7 shows the section of the power diagram we'll be working on, with components and connections made in this section in **RED**.

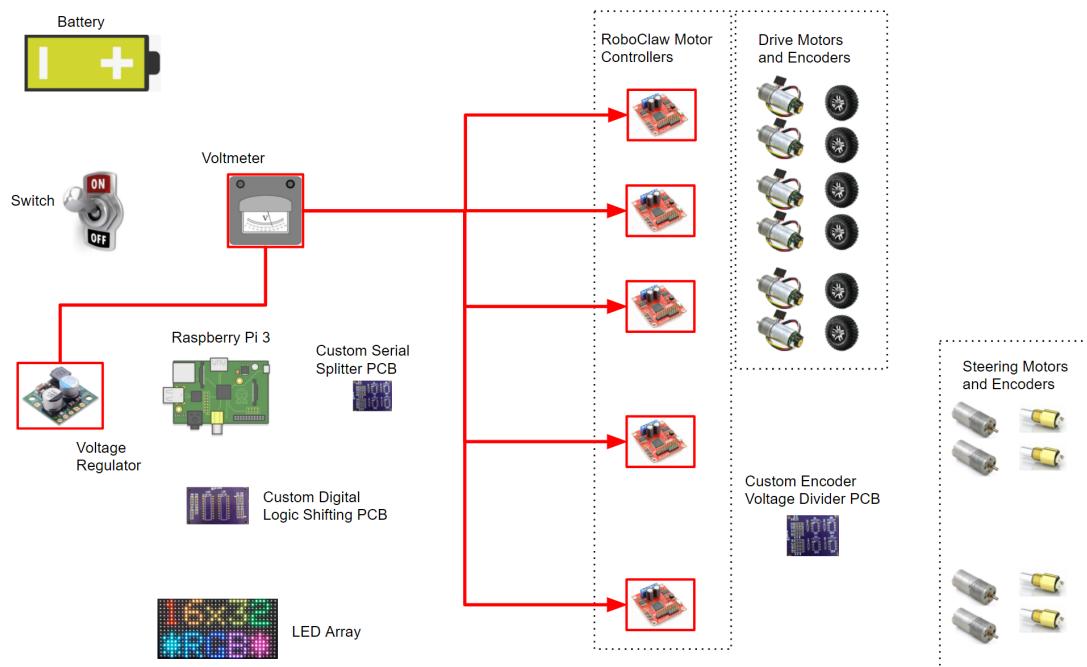


Figure 7: Regulator and Motor Controllers Overview

The "LOAD" terminals of the volt meter are the electrical load of the robot, which

will be all the electronics running in the robot. Figure 8 shows the pin-out of how to connect the volt meter to the regulator and the motor controllers.

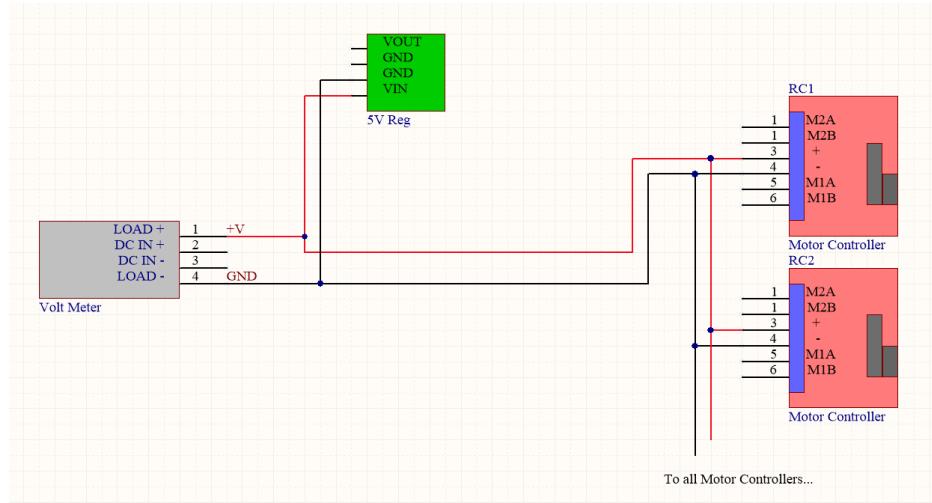


Figure 8: Volt Meter to Electronics connections

The LOAD+ pin should connect to VIN on the 5V Regulator, and + on each of the RoboClaw Motor Controllers, and the LOAD- pin should connect to GND on the Regulator and - on the RoboClaws. After the Volt Meter you should break out the connections to the regulator and RoboClaws into two separate wires, each with sufficient wire gauge. The 5V reg will be fine with 20AWG wire, but the one line running to every motor controller should be 16AWG.



Pololu 5A Step-Down Voltage Regulator D24V50Fx, top view with labeled pinout.

Figure 9: Voltage Regulator Diagram

Here in Figure 10 shows an example of one way we did the wire routing for power to the motor controllers. We can see that the power was split off before reaching any of the motor controllers, and instead each of them individually got a power and ground wire.

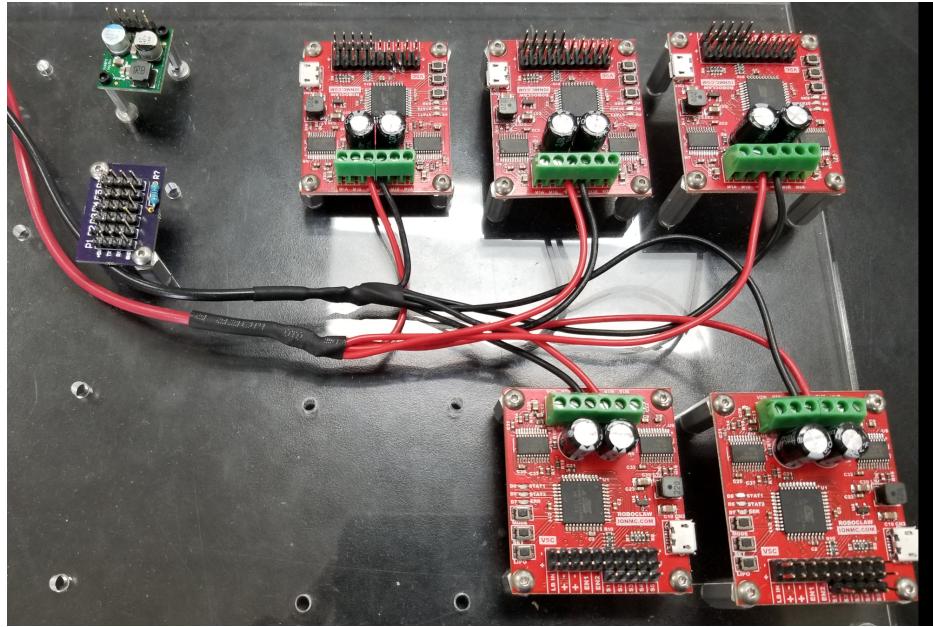


Figure 10: Powering the RoboClaws

Before connecting to the rest of the electronics we will want to test the voltage coming out of the regulators. To do this using a Multi-meter test across the for the 5V regulator on pins VOUT and GND, **Be very careful not to short across the GND and VOUT pins while testing** as this could short the regulator and cause it to break.

2.3 Powering the Raspberry Pi

Next we need to bring power to the Raspberry Pi. It requires a regulated 5V DC power source, so it will be powered from the 5V regulator. Figure 13 shows the section of the power diagram we'll be working on, with the power connections shown in **RED**.

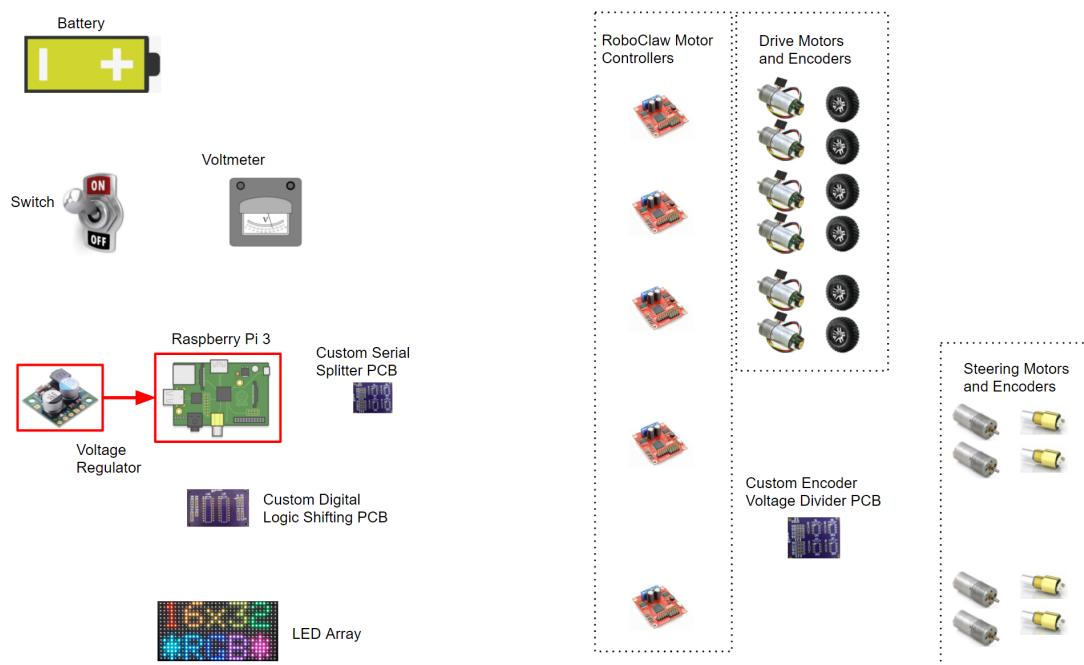


Figure 11: Powering the Raspberry Pi

Note: If you plan on using the LED matrix you should split 5V power off of the 5V regulator before the Raspberry Pi, and that should be done now. As the LED Matrix takes up a large number of GPIO pins which some might want for other devices it's not a required part of the project, and thus there is a separate document describing how to put it together.

The method we used to power the pi is soldering to the power pads on the bottom of the Raspberry Pi, the positive voltage goes to pad PP2 and negative/ground goes to pad PP5. For more information and a video on doing this you can follow this link and go to around 3:30

- "<https://www.youtube.com/watch?v=9LAtu39xpR8>" .

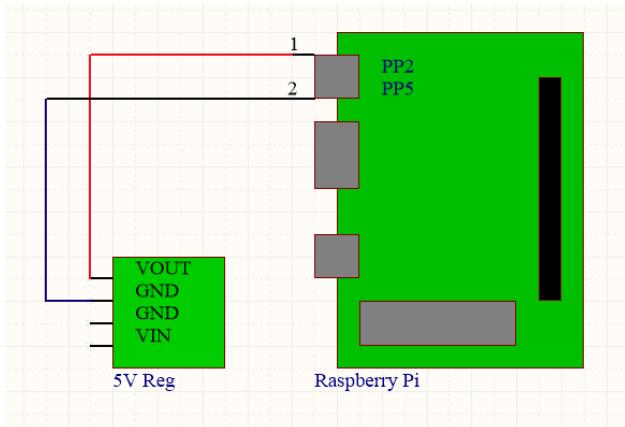


Figure 12: Raspberry Pi 3 soldering pads

2.4 Serial Communication

Connecting the Raspberry Pi to Serial Splitter Board: In order for the Raspberry Pi to talk to the motor controllers we will be using Serial communication. Figure 13 shows the section of the power diagram we'll be working on, with the power connections shown in **RED**, and data lines in **BLUE**.

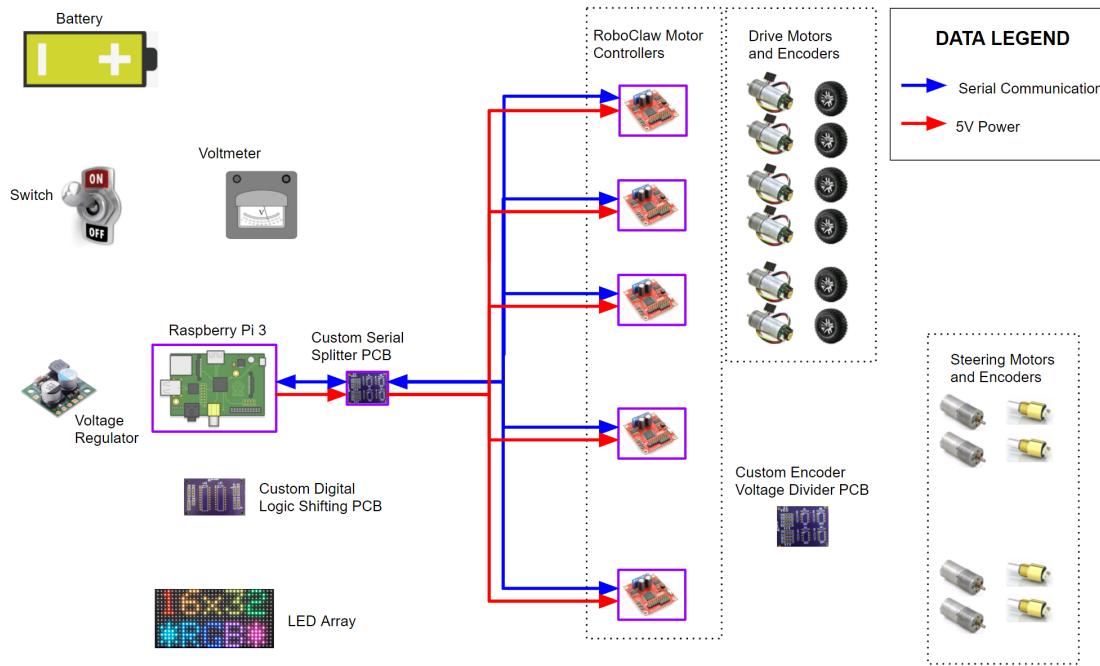


Figure 13: Serial Splitter Overview

Figure 14 shows the schematic and pin-out of how to connect the RPI, Serial Splitter board, and Motor Controllers. From the Raspberry Pi the pins we will use are going to be the UART TX and RX pins, which correspond to pins #8 and #10, or GPIO14 and GPIO15. In addition we will be passing 5V to the motor controllers for the logic battery controller which is used by the encoders and digital logic. For this use the 5V PWR rail, or pin #02 or #04, and any of the GND pins (we recommend pin #06). Raspberry Pi GPIO diagrams can be found on the following page in Figure 15

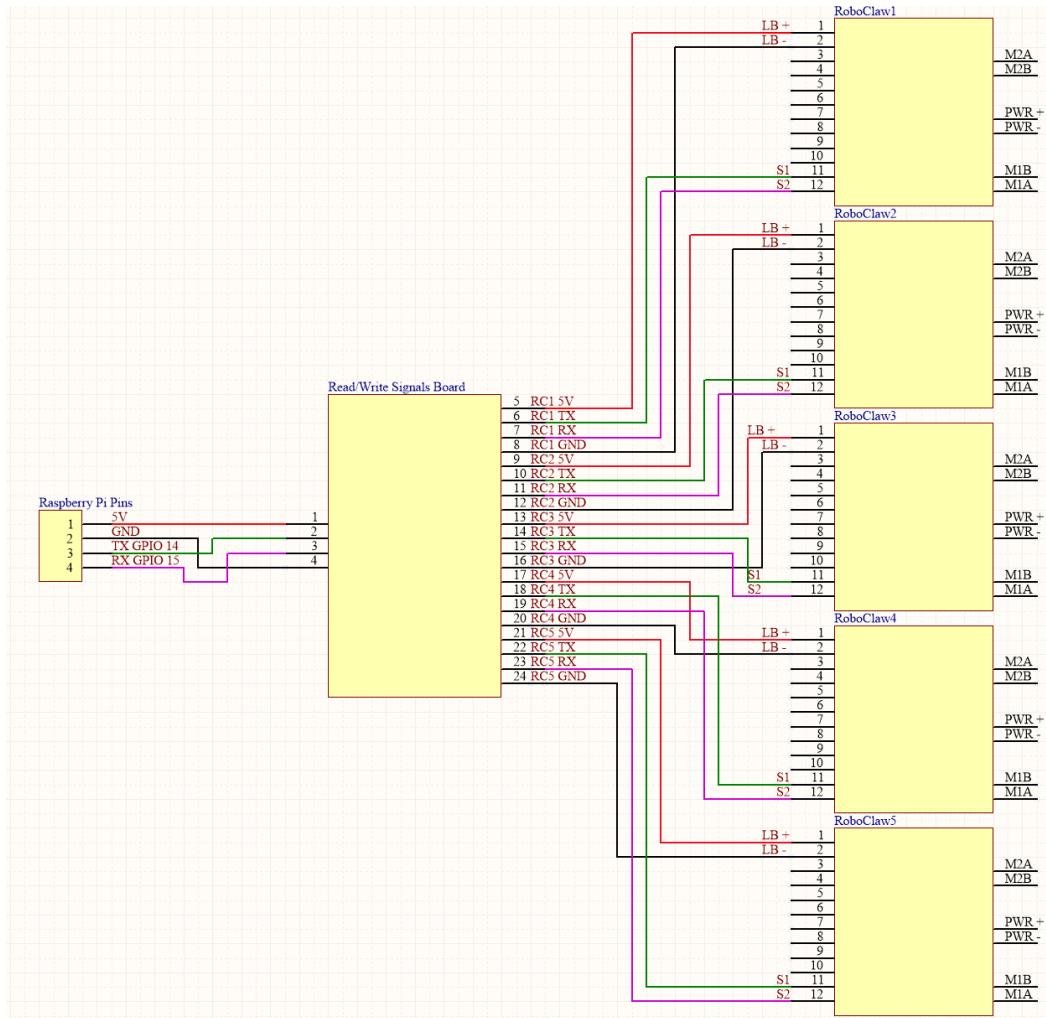


Figure 14: RPi connections to RoboClaws

Below shows the description of what each pin connects from and to on the Serial Splitter board. Use this in combination with Figure 14 and Figure 16 to make the serial connections to the RoboClaw Motor Controllers.

Pin	Description
1	+5V from Raspberry Pi 5V DC pin #2
2	Serial Write line, TX from Raspberry Pi GPIO 14
3	Serial Read line, RX from Raspberry Pi GPIO 15
4	GND from Raspberry Pi GND pin #6
5,9,13,17,21	5V to RoboClaws LB + pin
6,10,14,18,22	Serial Write to RoboClaws S1 pin
7,11,15,19,23	Serial Read to RoboClaws S2 pin
8,12,16,20,24	GND to RoboClaws LB - pin

Please note the difference between the pin labeling for the Raspberry Pi 3, and what the difference is between GPIO pin numbers, and the physical pin numbering. Consult Raspberry Pi forums and documentation if you are needing additional information

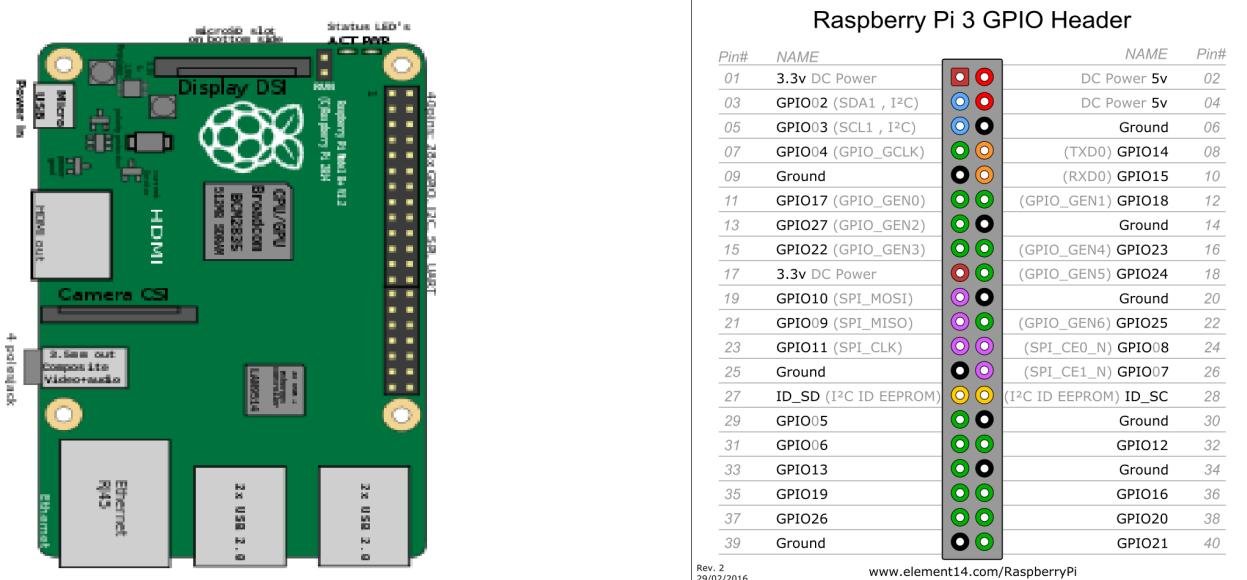


Figure 15: Raspberry Pi 3 pinout


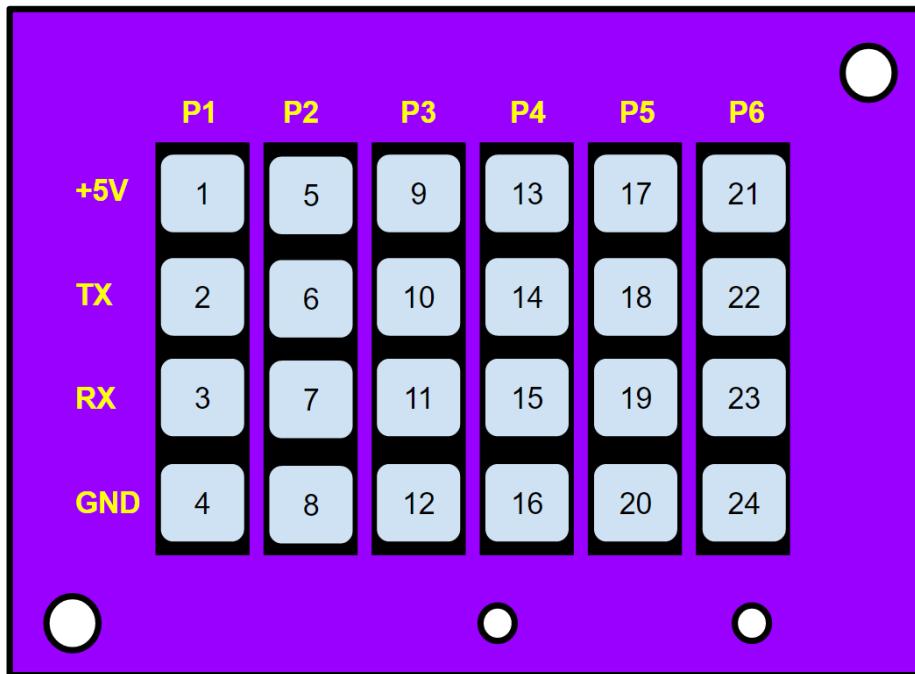


Figure 16: Read/Write Board

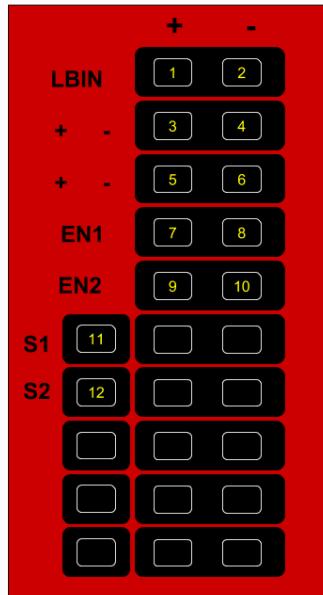

1. Logic Battery Power (+5V)
2. Logic Battery GND
3. Encoder 1 Power (+5V)
4. Encoder 1 GND
5. Encoder 2 Power (+5V)
6. Encoder 2 GND
7. Encoder 1 Signal (PWM signal A if quadrature encoder, 0-2V if absolute)
8. Encoder 1 Signal (PWM signal B if quadrature encoder, open if absolute)
9. Encoder 2 Signal (PWM signal A if quadrature encoder, 0-2V if absolute)
10. Encoder 2 Signal (PWM signal B if quadrature encoder, open if absolute)
11. Serial Read (TX line from Raspberry Pi)
12. Serial Write (RX line from Raspberry Pi)

Figure 17: RC pinout

Next following Figure 14 and the pinout Figures 16 and 17 connect the signals out to

each individual RoboClaw². For more information on the pins for the RoboClaws and their purpose refer to the RoboClaw Manual and data sheet.

Examples of the wiring and routing can be seen in Figure 18 and Figure 21

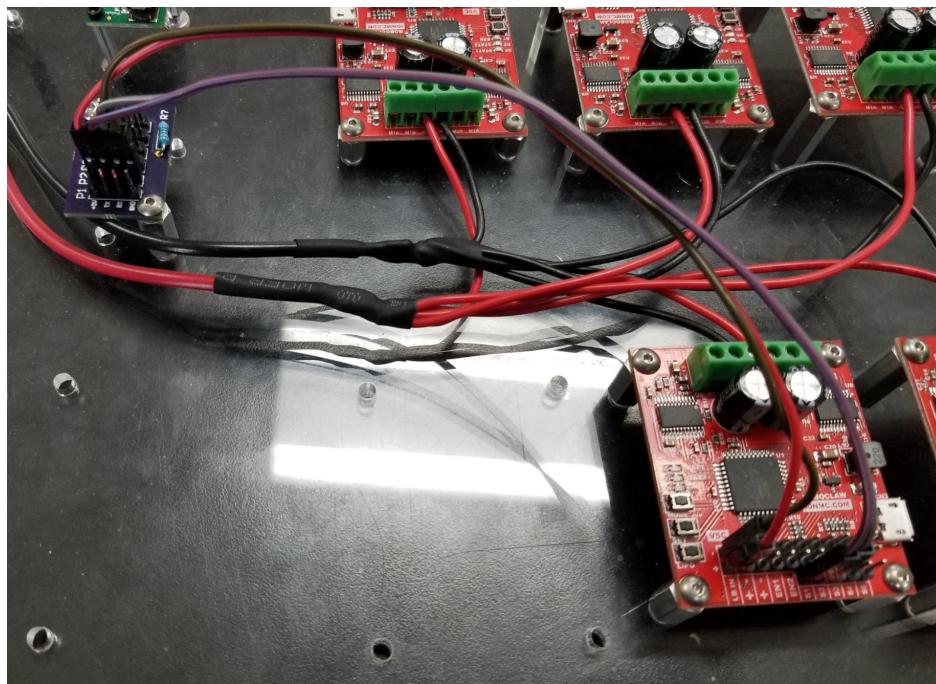


Figure 18: Serial Splitter to RoboClaws

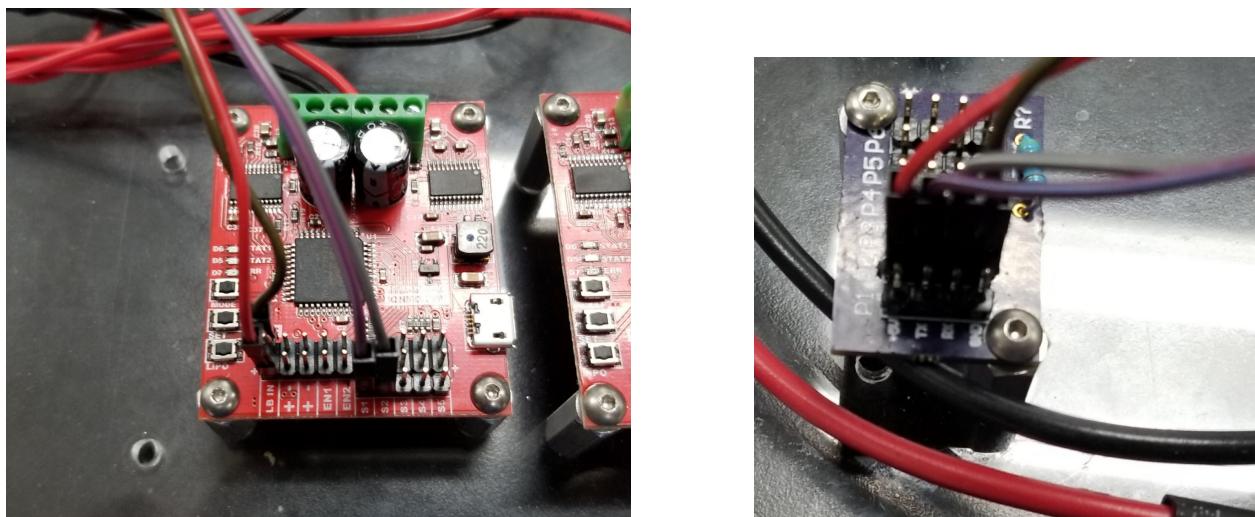


Figure 19: Serial signal routing

²The pin number in Figure 14 for the Serial Splitter Board corresponds to the pin numbers in Figure 16

3 Connecting Motors/Encoders

Next we can connect the Motors and encoders to the RoboClaw Motor Controllers. For each of the 10 motors you will need to be connecting motor power, as well as the encoders. This means that there will be Close to 60 Wires being routed between the motor controllers and motors/encoders, and it is important to try to keep your wires organized and bundled together well. Below is some learning information about strain relief and using wire braid in your electronics system.

- <https://www.techopedia.com/definition/2301/strain-relief>
- <https://www.youtube.com/watch?v=FeCs98TSsYQ>

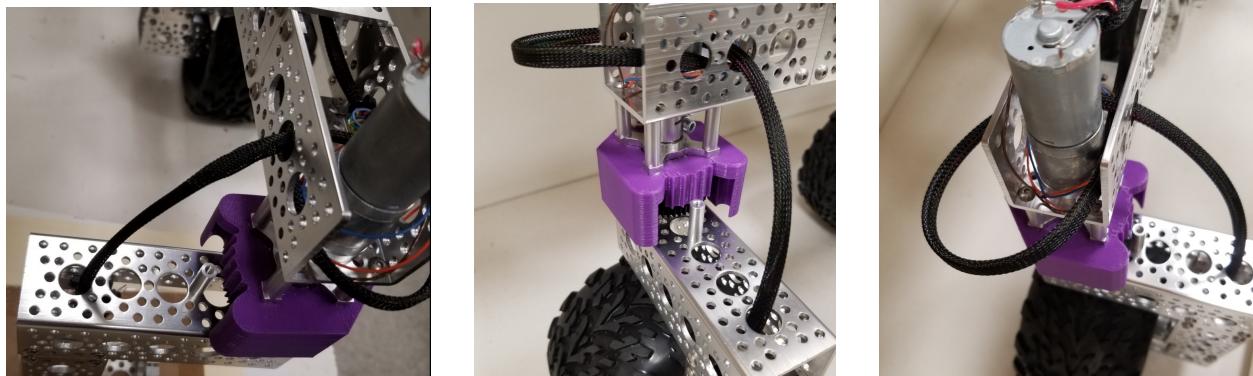


Figure 20

An example of how we routed our wiring is shown by Figure 20. It is important to give strain relief in the cable as you are routing it through as you can see from our example, as well as giving extra wiring for the locations that can move. In addition Figure ?? shows how we routed the wires through the rocker-bogie, and then from the rocker-bogie into the main body. Try to pick locations of routing into the body that reduce strain on the wires as the robot legs move.

3 CONNECTING MOTORS/ENCODERS



Figure 21: Serial signal routing

Section	Wires Needed	Length [inches]
A	2x 24AWG & 4x 30AWG	??
B	2x 24AWG & 4x 30AWG	??
C	2x 24AWG & 4x 30AWG	??
D	2x 24AWG & 3x 30AWG	??
E	2x 24AWG & 3x 30AWG	??

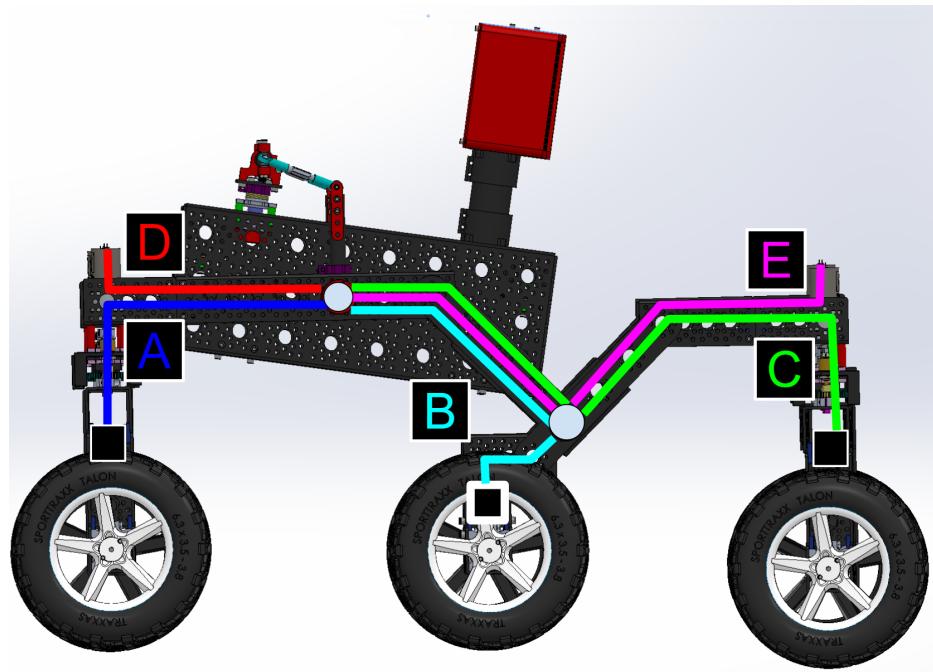


Figure 22: Wire labels

3.1 Drive Motors

At this point we want to connect our motors to the motor controllers, we will begin with the drive motors (the 6 motors at each of the bottom of the wheels). Figure 23 shows the section of the power diagram we'll be working on, with lines with both encoder signals and motor power in **PURPLE**.

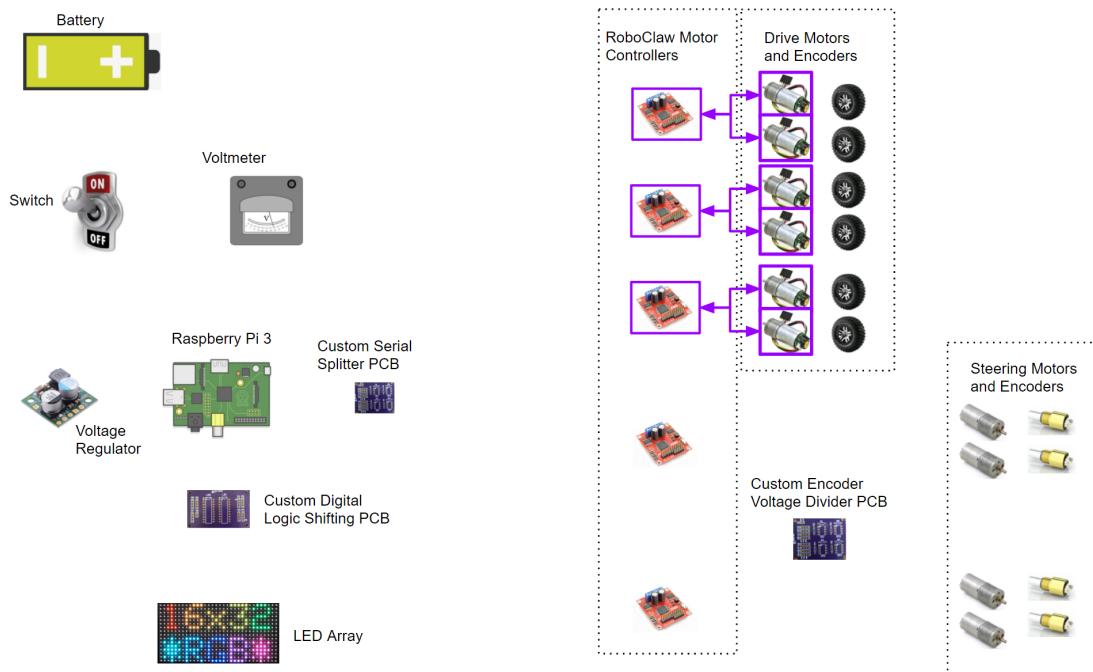


Figure 23: Motor and Encoder Overview

Make sure to look at which RoboClaw corresponds to which motors it is controlling. It is important that this ordering is preserved. Assign and mark each of your RoboClaws a number 1-5 and then follow Figure 24 when connecting each to its' motors.

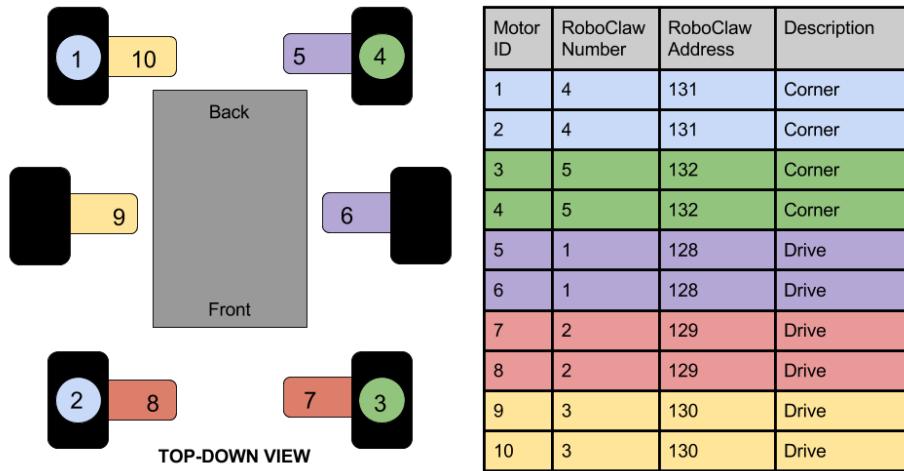


Figure 24: RoboClaw - Motor Assignments

Figure 25 shows what each socket in the connector to the motor goes to, and Figure 26 shows which of those should connect to what pin on the RoboClaw motor controllers. Note that the white wire is represented by pink in the diagram.³

Color	Function
Red	motor power (connects to one motor terminal)
Black	motor power (connects to the other motor terminal)
Green	encoder GND
Blue	encoder Vcc (3.5 – 20 V)
Yellow	encoder A output
White	encoder B output

Figure 25: Motor pinout

³Figure 26 shows only a single motor controller and 2 motors, broken into 2 pictures to reduce clutter on the image and increase wire readability.

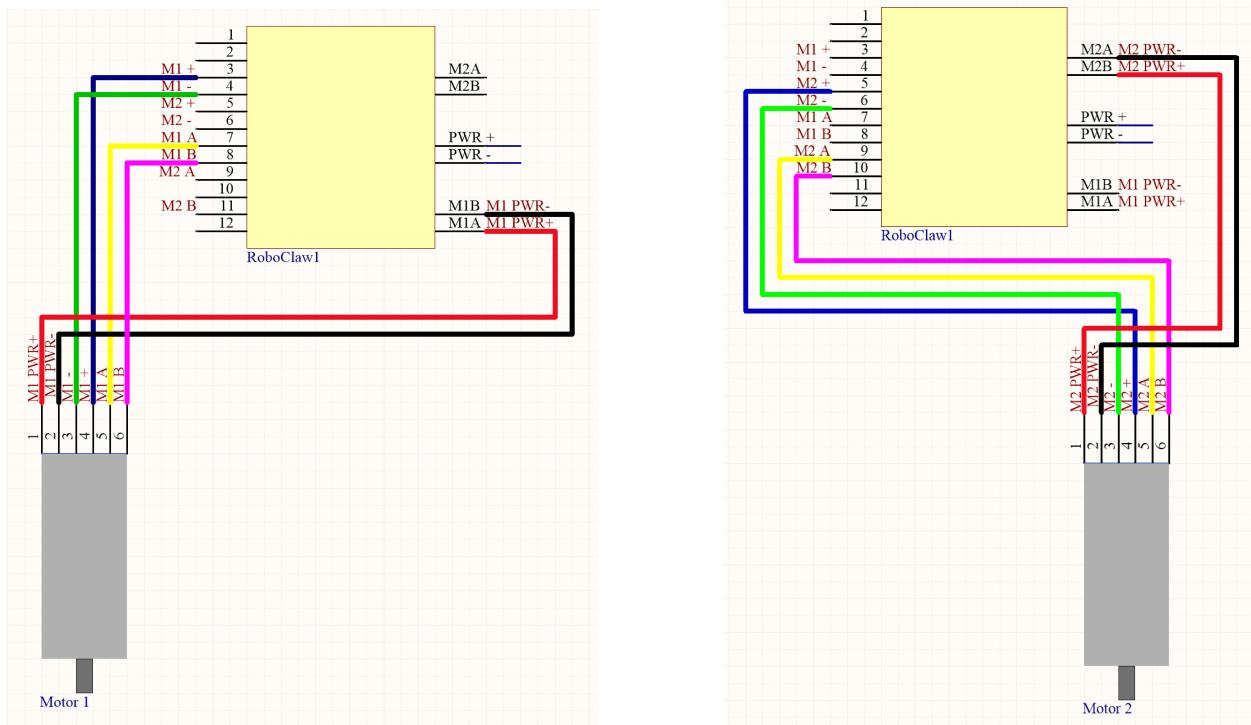


Figure 26: Connecting RoboClaws to Drive Motors

3.2 Corner Motors/Encoders

The big difference between the corner motors and drive motors is the use of absolute encoders. These are encoders that are separate from the motor and so we have to do a little bit of work to get them to interface into the Motor Controllers well. Figure 27 shows the section of the power diagram we'll be working on, with lines that power the motors in **RED**, and encoder signals in **BLUE**.

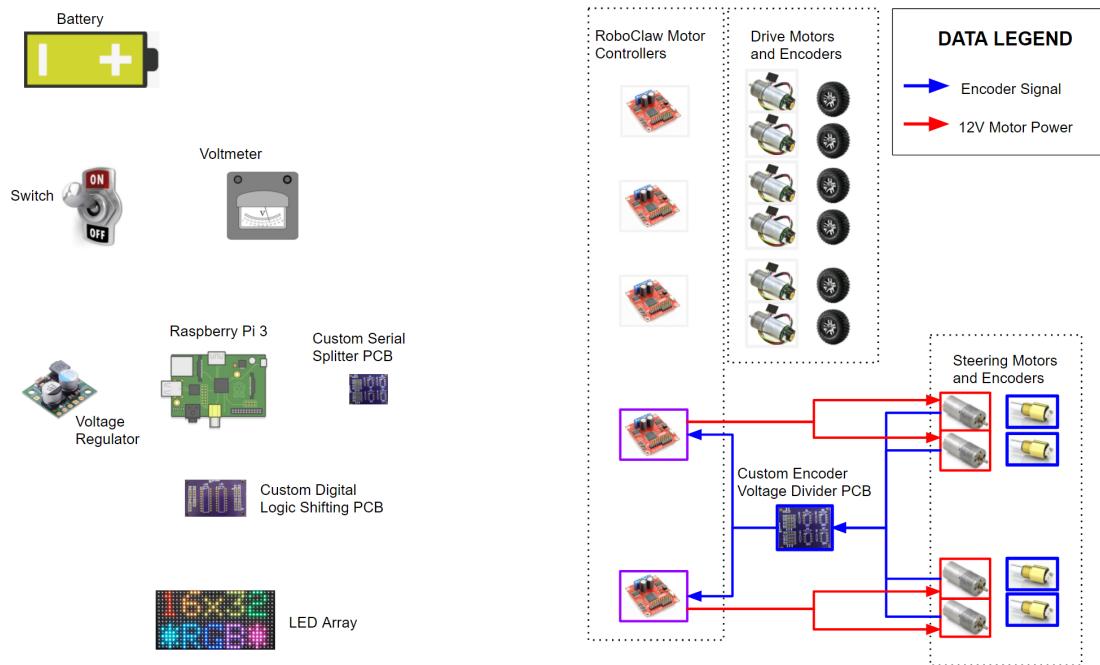


Figure 27: Corner Motor and Encoder Overview

The corner motors only have the two connections to the physical motor, the (+) and (-) going to the top of the motor, however you must also hook up the Absolute encoder. When plugged in the encoder the 3-pin Micro connector will have 3 wires coming out of it, shown in Figure 28.

Pin	Description	Color
1	+5V DC Power	Orange
2	0-5V Analog	Blue
3	Ground	Brown

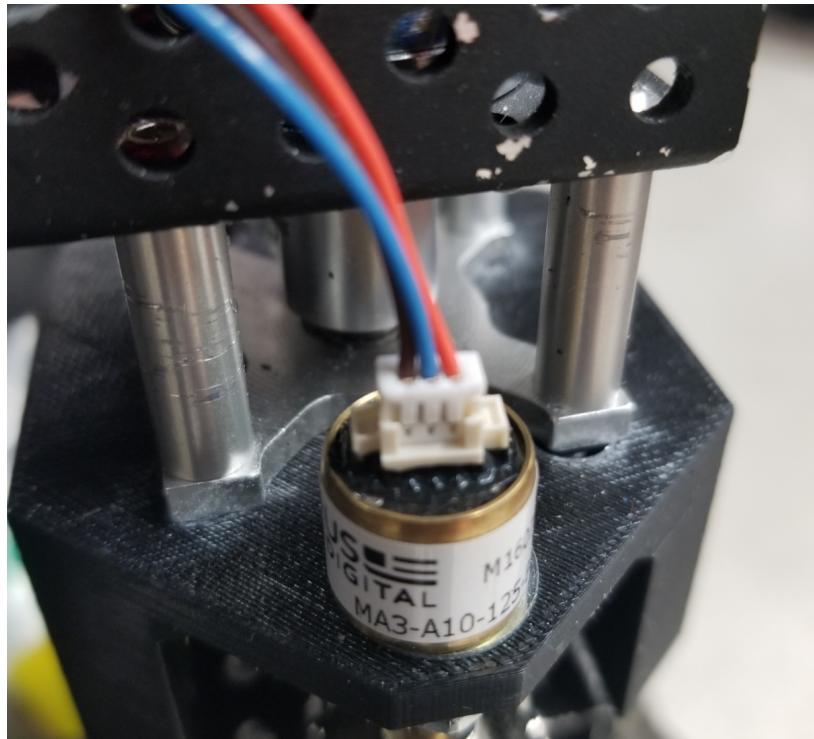


Figure 28: 3-pin Micro connector

The absolute encoder will be hooked up similarly to the encoders for the drive motor on the RoboClaw side, with the exception of the OUTPUT B signal which doesn't exist for absolute encoder types, it just needs to send the 10-Bit analog signal to the RoboClaw. However there is an issue where the encoder outputs signals on a 0-5V scale, but the RoboClaw expects an input of 0-2V for an absolute encoder value. For this we will use the Encoder Voltage Divider PCB, the pinout of which can be seen in Figure 29.

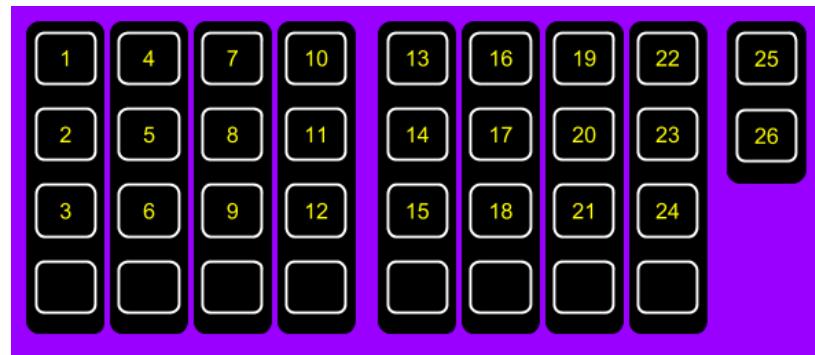


Figure 29: Encoder Voltage Divider board pinout

Pin	Description
1,4,7,10	+5V Input to Encoders
2,5,8,11	0-5V Signal from Encoders based on position
3,6,9,12	GND for Encoders
13,16,19,22	+5V Power from each respective RoboClaw
14,17,20,23	0-2V Signal Output to RoboClaws, after voltage division on board
15,18,21,24	GND from each respective RoboClaw
25	+5V from Raspberry Pi power rail
26	GND from Raspberry Pi pin

4 CONNECTING THE LED MATRIX

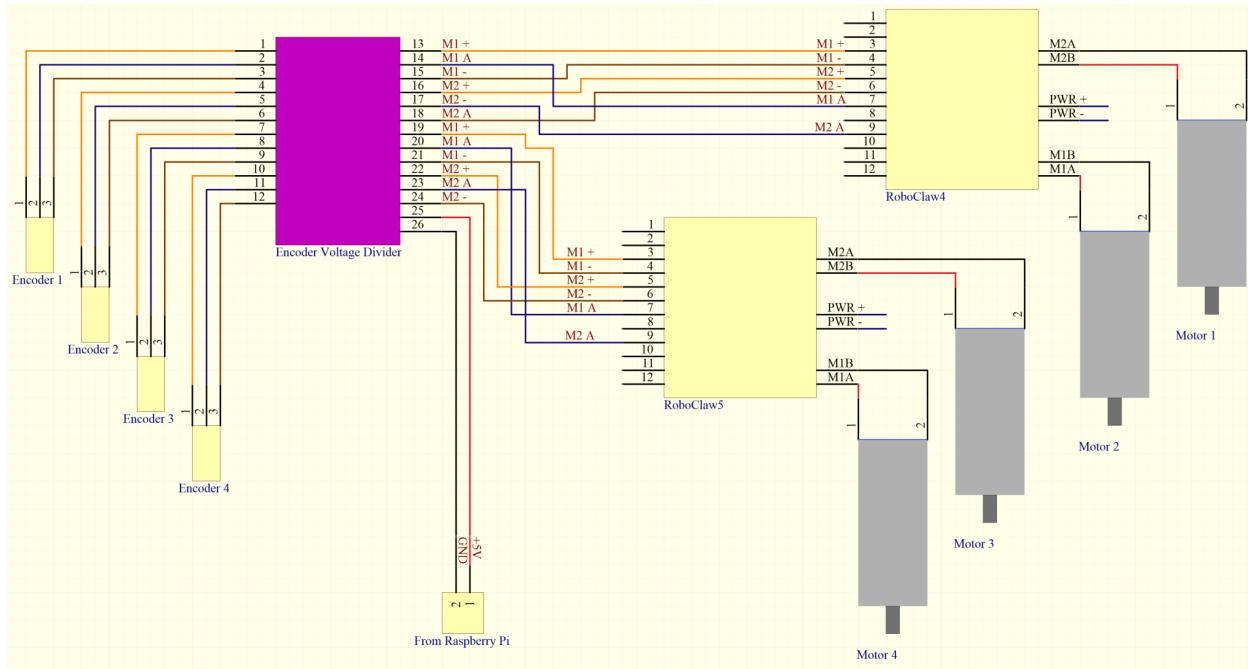


Figure 30: Connecting RoboClaws to Corner Motors

Once all 10 of the motors are connected in the system we are ready to move onto the Motor tuning and calibration process, in the Calibration.PDF. Make sure to double check all your wire connections and that they are into the correct pins before moving on. We recommend doing this and having the robot functioning before moving on to the LED Matrix, though either order would be fine.

4 Connecting the LED Matrix

We followed along with a project on Adafruit to hook up the Raspberry Pi to the LED matrix, with the addition of the logic shifter board inbetween the Pi and LED matrix. It can be found at:

- <https://learn.adafruit.com/connecting-a-16x32-rgb-led-matrix-panel-to-a-raspberry-pi/overview>

Figure 31 shows an overview of how the logic shifters are used inbetween the signals from the Raspberry Pi to the LED Matrix. This does not have the pin connectors to the Logic Shifter board in it, it is just to demonstrate the signal path.

4 CONNECTING THE LED MATRIX

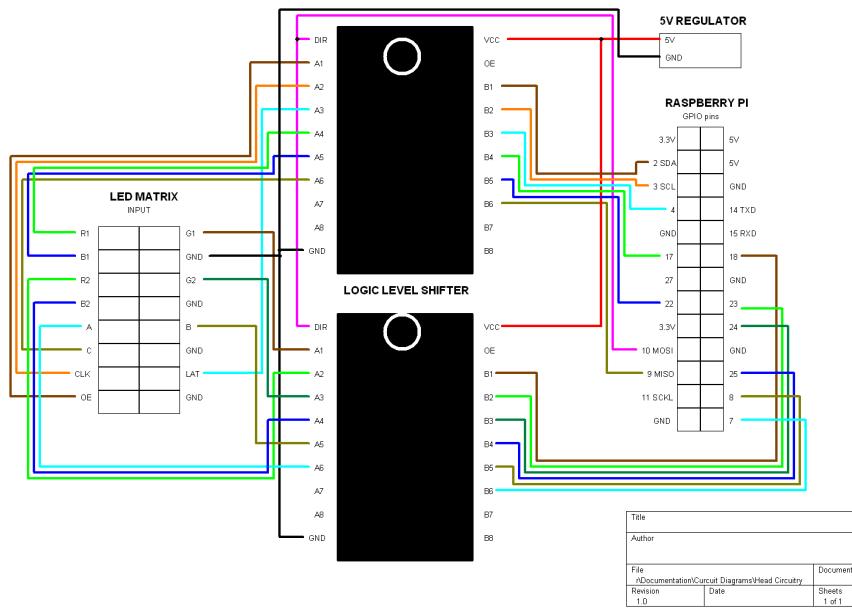


Figure 31: Raspberry Pi connections to LED Matrix

The Logic Shifter PCB is not included in the adafruit project, the following will be descriptions as to how to include that in the wiring and routing. Figure 32 shows the pin connections on the Logic shifter, labeled with which pin they connect to on the Raspberry Pi. We suggest putting the logic shifter board in the 3D printed head, and routing the wires through the body and up through the pvp pipe "neck".

Make sure to use the thicker gauge wire (20AWG) for powering the LED matrix, as it can pull up to 5 amps of current, we want to make sure to use wire thick enough for it, however all the other signals are digital signals which the 30 AWG wire is fine for.

4 CONNECTING THE LED MATRIX

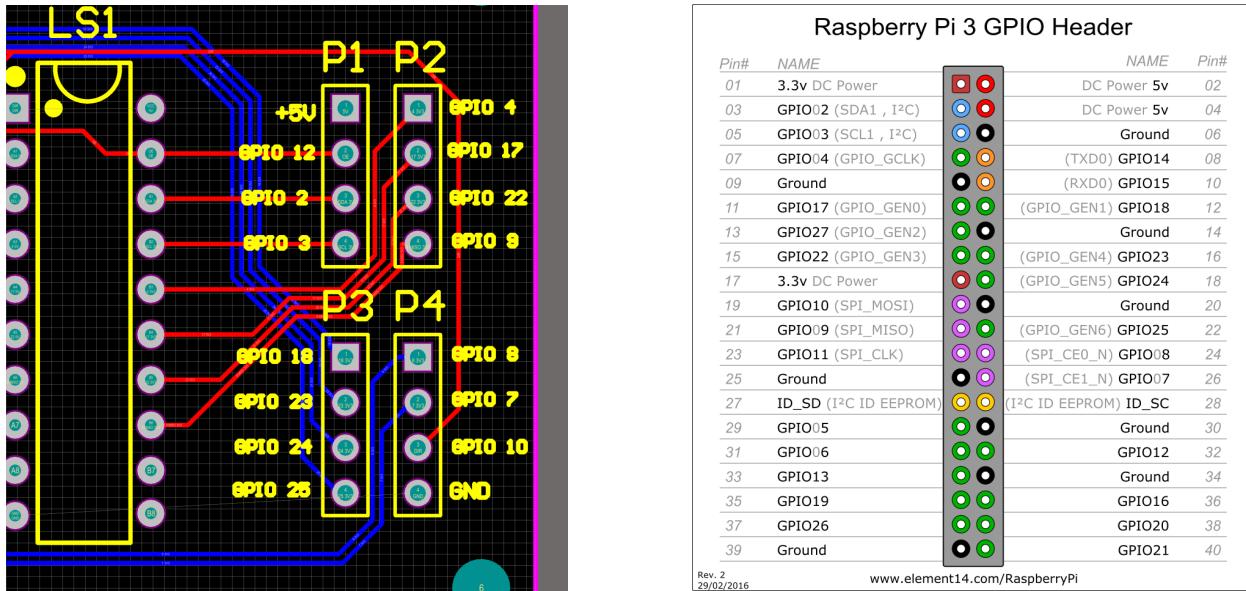


Figure 32: Raspberry pi to Logic Shifter board

****Note**** In Figure 32 the pin labels on the board (left) correspond to the pin NAME not the pin number. So pin 12 is the pin NAME GPIO 12, and **Not** pin#12

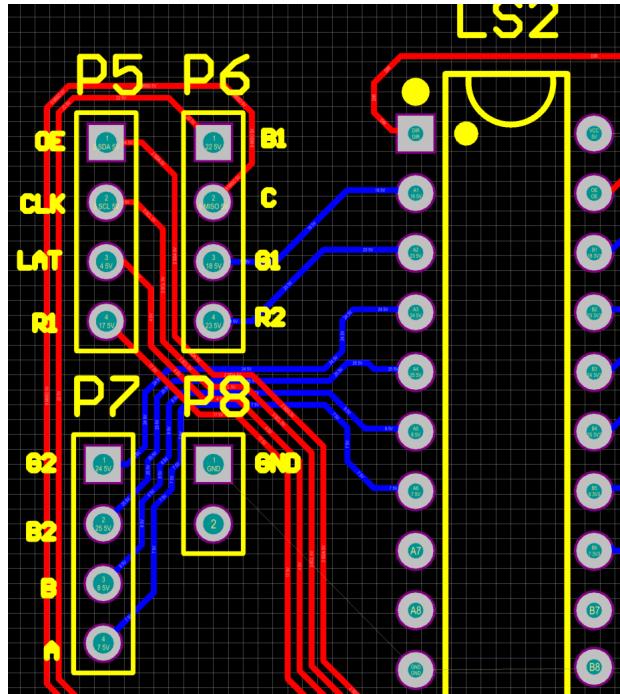


Figure 33: Logic Shifter to LED Matrix

Figure 33 shows the connections out of the Logic Shifter board to the LED Matrix.

4 CONNECTING THE LED MATRIX

Make sure to use the INPUT side of the LED matrix. Labels of the pin namings can be found directly on the LED Matrix.